

---

---


# EE 394V: ANALYSIS OF POWER SYSTEMS WITH RENEWABLE ENERGY SOURCES

## FINAL PROJECT: DISTRIBUTION CIRCUIT MODELING FOR HARMONICS

Soham Roy and Fernando Osorio
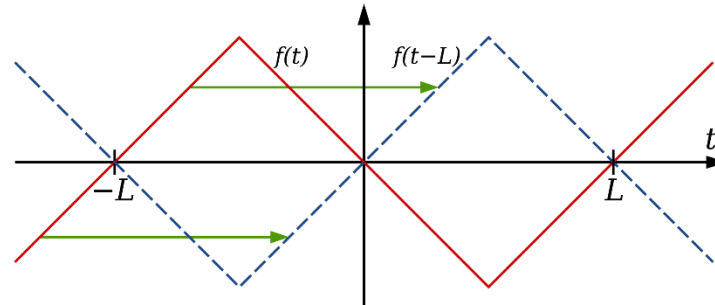
# Motivation


- Non-linear loads and inverter-based generation (e.g. solar PVs) in distribution grid
- Harmonics (3<sup>rd</sup>, 5<sup>th</sup>, 7<sup>th</sup>...) produced by power electronic devices (i.e. rectifiers, inverters, VFDs)
  - Elements of the Fourier series of any periodic signal
  - Occur at multiples ( $h \times f_1$ ) of the fundamental frequency ( $f_1$ )
  - Even order harmonics (2<sup>nd</sup>, 4<sup>th</sup>, 6<sup>th</sup>...) usually absent due to half-wave symmetric waveforms:  $f(t) = -f(t - L)$



Half-wave symmetric waveform [1]

- Distribution circuit models can be expanded to incorporate harmonics

# Background: Fundamentals of Harmonics

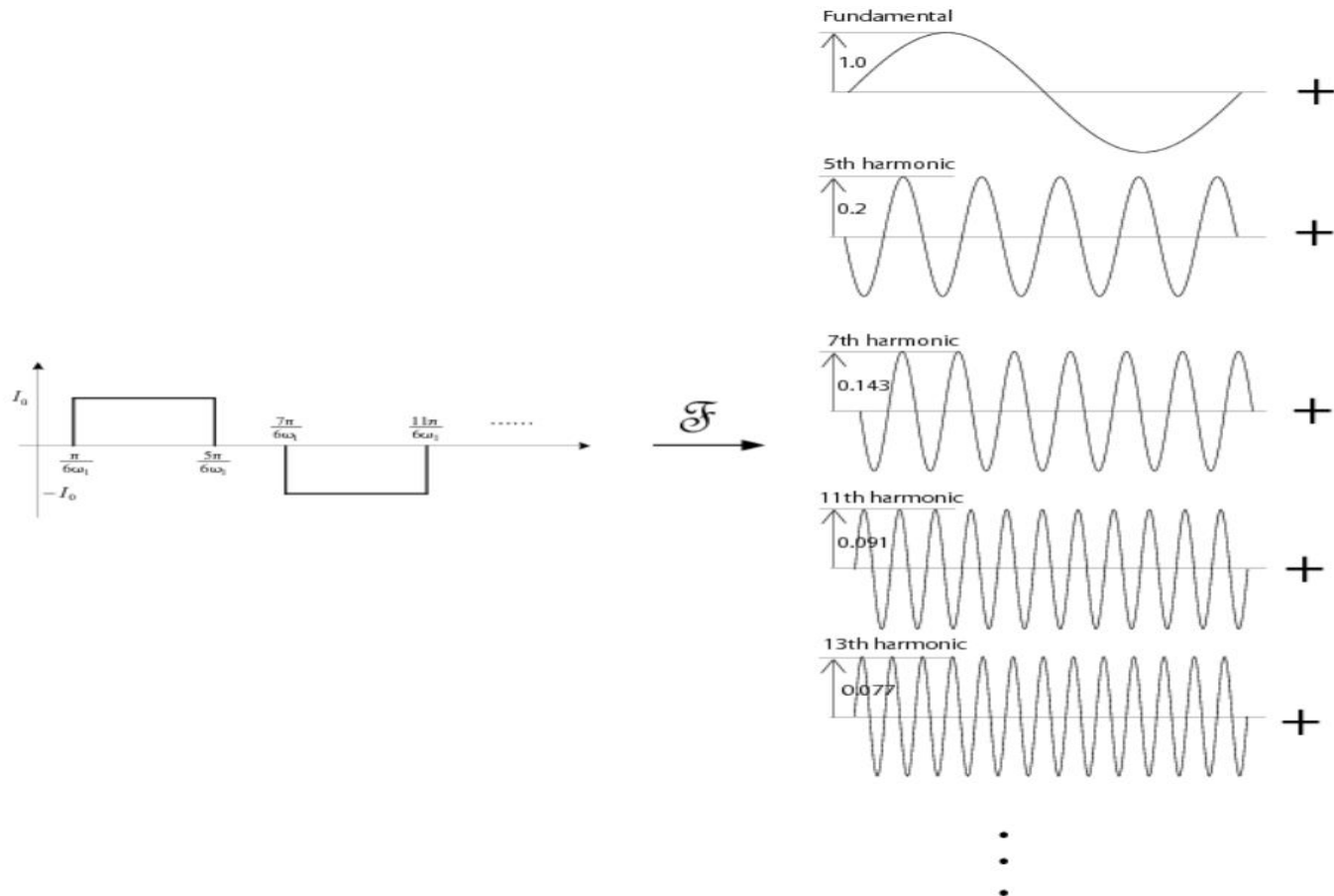

**6-pulse Full Bridge Rectifier: non-sinusoidal current waveform is decomposed into its Fourier series. Harmonic currents are constituent of the Fourier series [2]**

# Background: Harmonic phase sequences for 3-phase balanced power system [2]

$$i_a(t) = \sum_{h=1,2,3}^{\infty} I_h \sin(h\omega_1 t + \theta_h)$$

$$i_b(t) = \sum_{h=1,2,3}^{\infty} I_h \sin\left(h\omega_1 t + \theta_h - h\frac{2\pi}{3}\right)$$


$$i_c(t) = \sum_{h=1,2,3}^{\infty} I_h \sin\left(h\omega_1 t + \theta_h + h\frac{2\pi}{3}\right)$$

Harmonic order	Phase sequence	Harmonic order	Phase sequence	Harmonic order	Phase sequence
1	+	7	+	13	+
2	-	8	-	14	-
3	0	9	0	15	0
4	+	10	+	16	+
5	-	11	-	17	-
6	0	12	0	18	0

Triplen (3<sup>rd</sup>, 6<sup>th</sup>, 9<sup>th</sup>...) harmonics have zero sequence behavior and add up in the neutral of a balanced power system
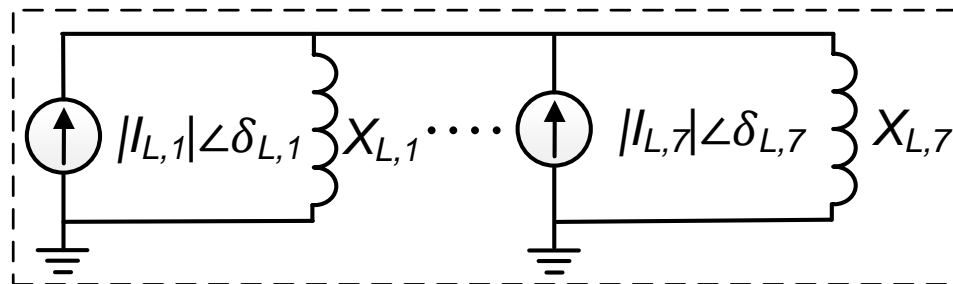
# Background: Current Source Model (CSM) for harmonics

- Non-linear loads and renewable energy sources: modeled using current source models (CSMs) to represent power electronics
- CSM reads current spectrum data and injects current
- Harmonic Norton equivalent impedances:
  - Challenging to compute
  - Usually very large; represented as open circuit to simplify simulations




CSM for harmonic source

# Objective


- Expand distribution line and transformer models in MATLAB to include harmonics:  $Y_{prim_{line}(h)}$  and  $Y_{prim_{xfmr}(h)}$
- Validate using OpenDSS and steady-state simulations in EMTP-RV

Three-phase transformer diagrams [2]



Grounded wye-  
grounded wye  
(Yg-Yg)

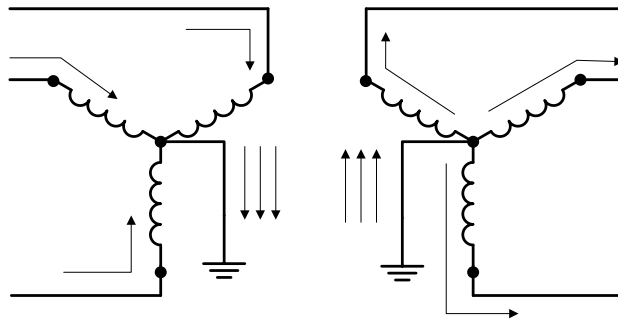

Grounded wye-  
delta (Yg-D)

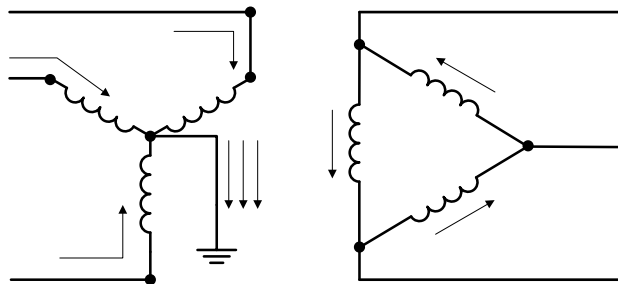

Winding diagrams

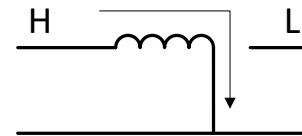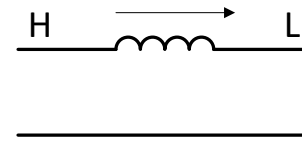

Zero Sequence Connections

# MATLAB Approach: Obtaining Ybus for harmonics and LF solution

## Distribution lines:

- Replace  $(R + jX)$  by  $(R + jhX)$  in  $\hat{Z}$  matrix to obtain  $\hat{Z}_{(h)}$
- No change in  $A$  matrix
- Obtain  $Y_{prim_{line}(h)} = A^T (\hat{Z}_{(h)} l)^{-1} A$

$\hat{Z}_{(h)}$  : harmonic phase impedance matrix

## Distribution Xfmr:

- Replace  $Z = R + jX$  by  $Z_{(h)} = R + jhX$ ; accordingly  $Z_{b(h)}$  is obtained
- No change in  $A$ ,  $B$  and  $N$  matrices
- Calculate  $Y_{1(h)} = B(Z_{b(h)})^{-1} B^T$  and  $Y_{w(h)} = N Y_{1(h)} N^T$
- Obtain  $Y_{prim_{xfmr}(h)} = A Y_{w(h)} A^T$

$Z_{(h)}$  : harmonic impedances

$Z_{b(h)}$  : harmonic impedance matrix

$Y_{1(h)}$ : harmonic nodal primitive matrix

$Y_{w(h)}$ : harmonic winding admittance matrix

Ybus:  $Y_{bus(h)}$  is obtained by appropriately combining  $Y_{prim_{line}(h)}$  and  $Y_{prim_{xfmr}(h)}$  for each harmonic frequency

## Multifrequency load flow (LF) analysis for harmonics [3]:

$I_{(h)} = Y_{bus(h)} V_{(h)}$  using H-bus method

# OpenDSS Approach: Harmonic LF solution

---

New "Spectrum.Spectrum\_Load\_a" NumHarm=4 CSVFile=Spectrum\_Load\_a.csv

	A	B	C
1	1	100	-58.8314
2	3	65.7	-162.494
3	5	37.7	84.8432
4	7	12.7	-39.8196

!Non-linear load

New Load.Non\_linear\_load bus=n4.1.2.3 Phases=3 conn=wye Kv=4.16

Kva=421.5119 Model=5 spectrum=Spectrum\_load\_a

Set neglectloadY=yes

!Solve without harmonics

solve




!Solve with harmonics

set mode=harmonics

solve


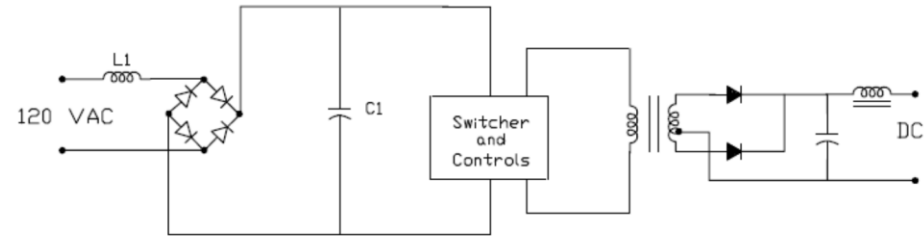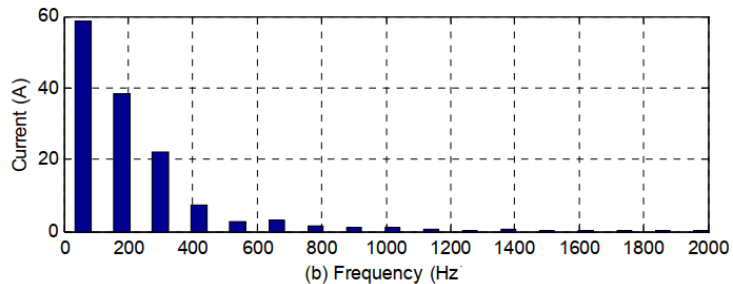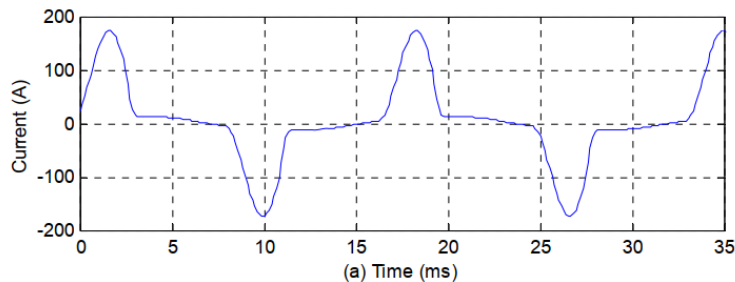
# Case study: Spectrum for CSM of non-linear Load [2]




h	% of IRMS [A]	Phase [deg]
1	100	-28
3	65.7	-71
5	37.7	-123
7	12.7	173

Fundamental current (rms): 58.5 A

Fundamental frequency: 60 Hz



Fundamental voltage: 120 V
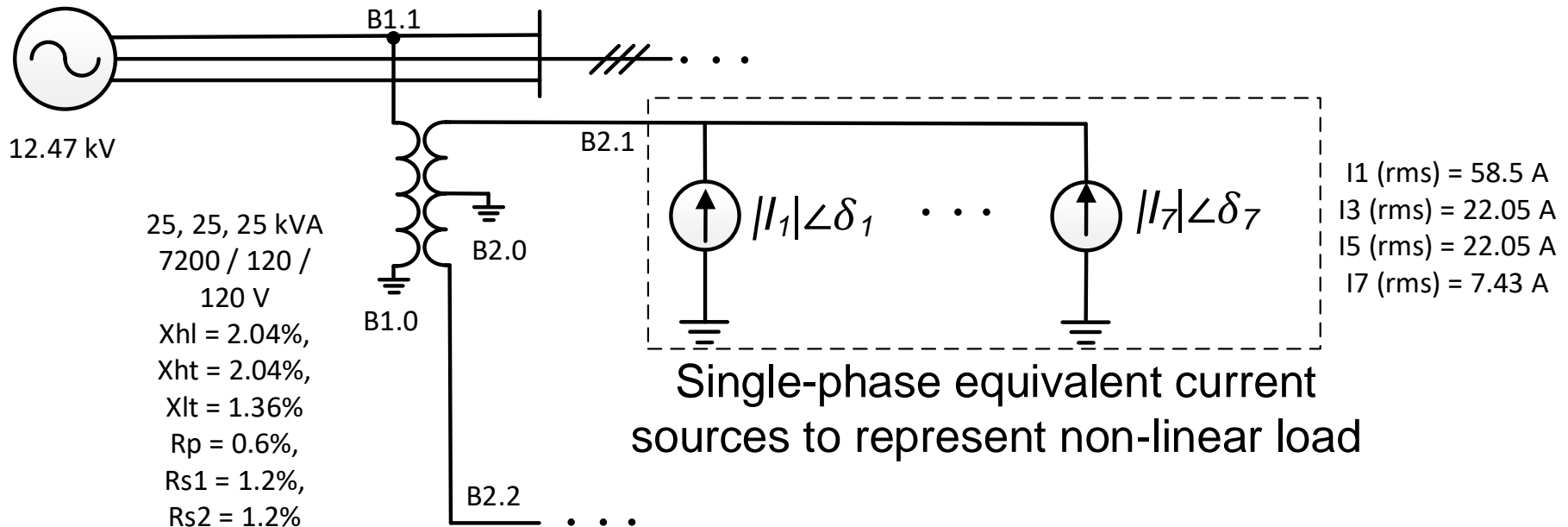
# Case study A: 7.2kV/120V/120V Center-tapped transformer





# Case study A: 7.2kV/120V/120V Center-tapped transformer

---

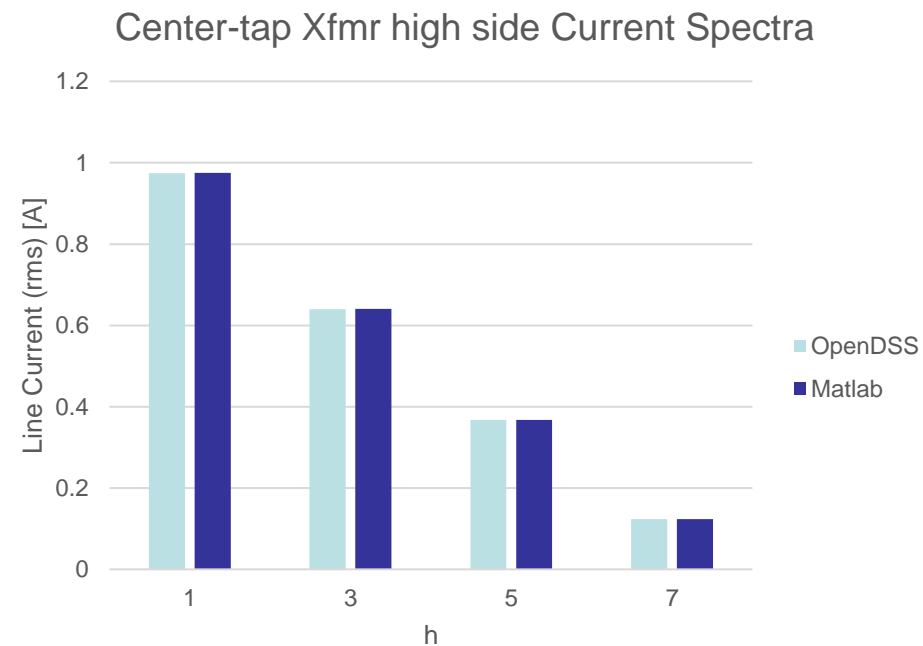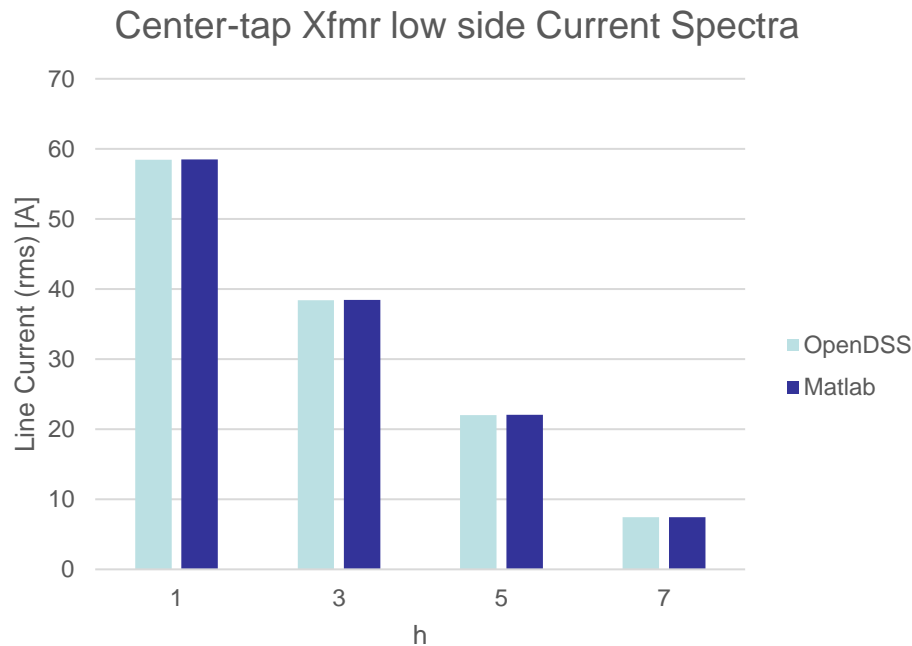

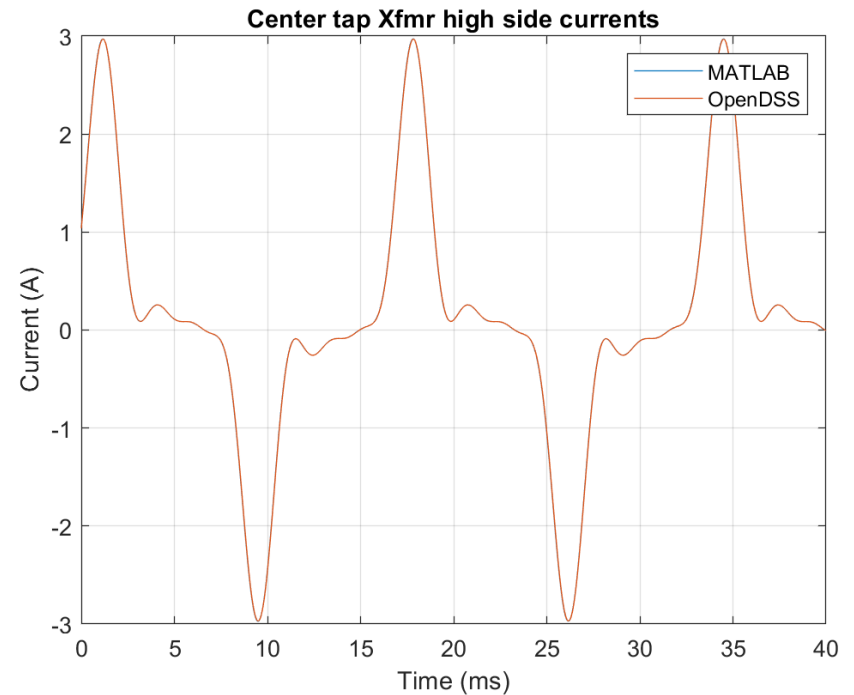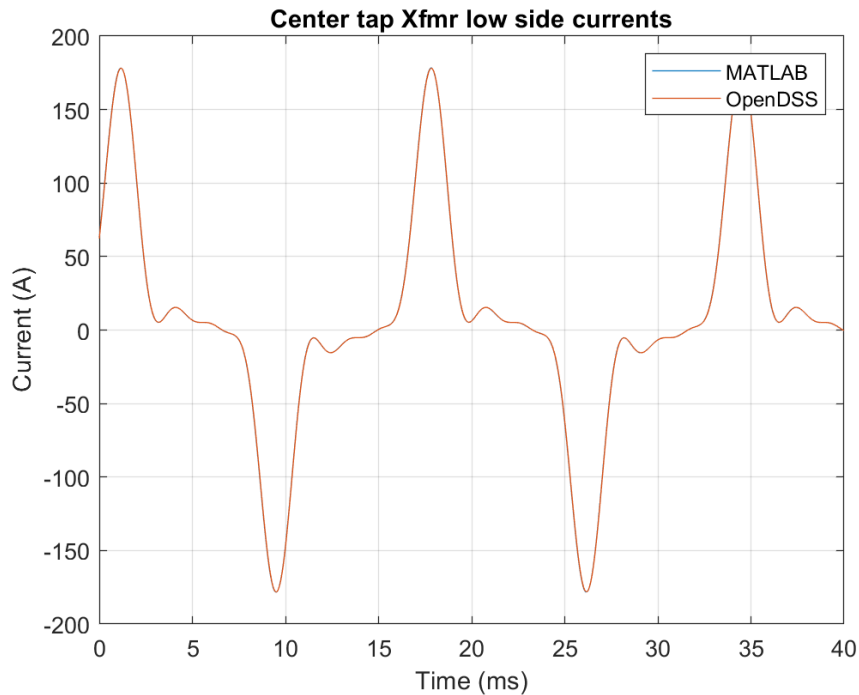
# Case study A: 7.2kV/120V/120V Center-tapped transformer




# Case study A: 7.2kV/120V/120V Center-tapped transformer


Center-tap Xfmr low side Voltage Spectra

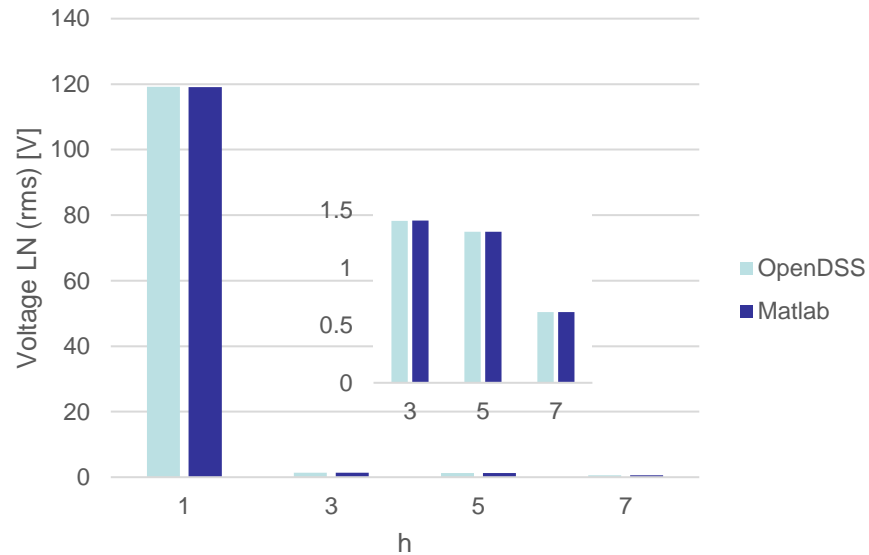


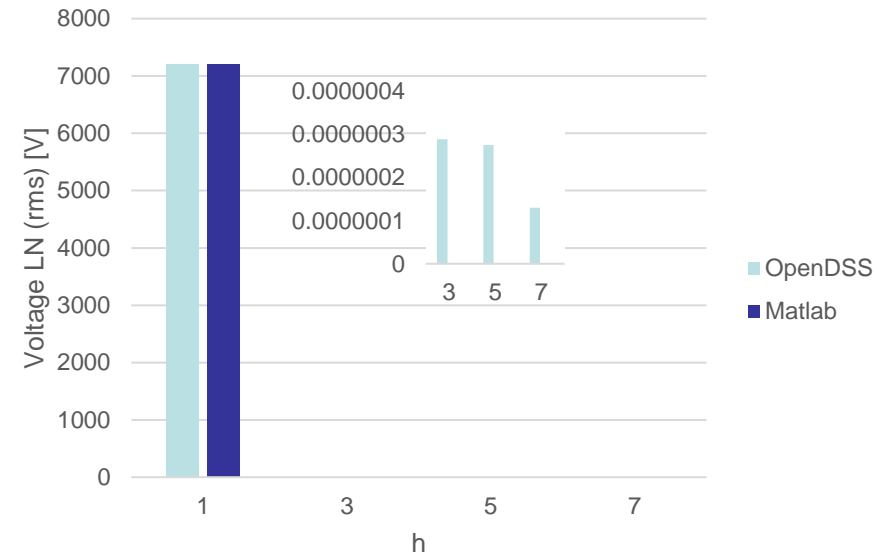
Center-tap Xfmr high side Voltage Spectra




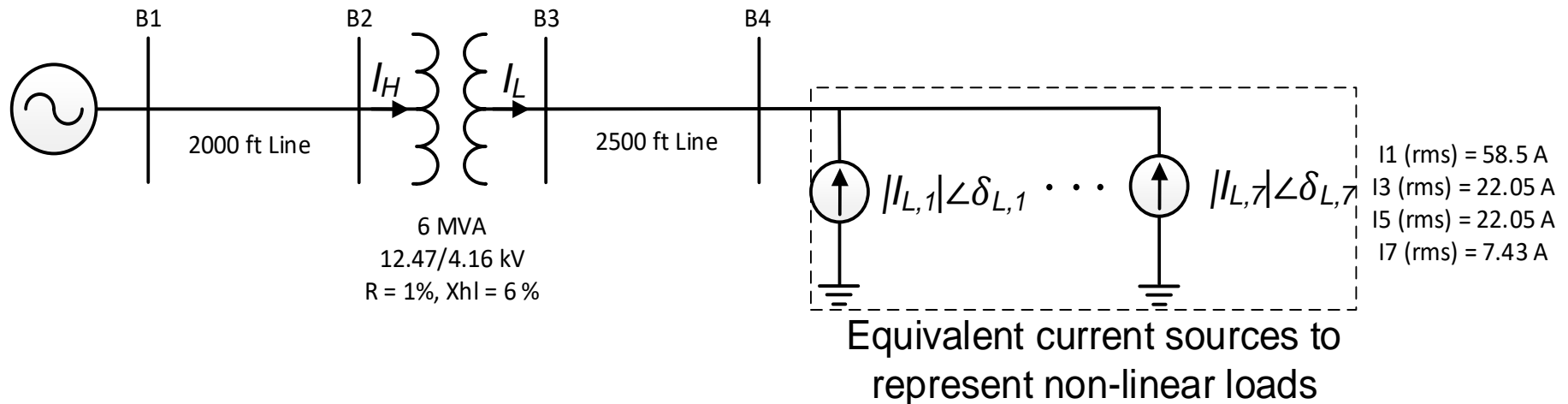
# Case study B: IEEE 4 bus system with non-linear load


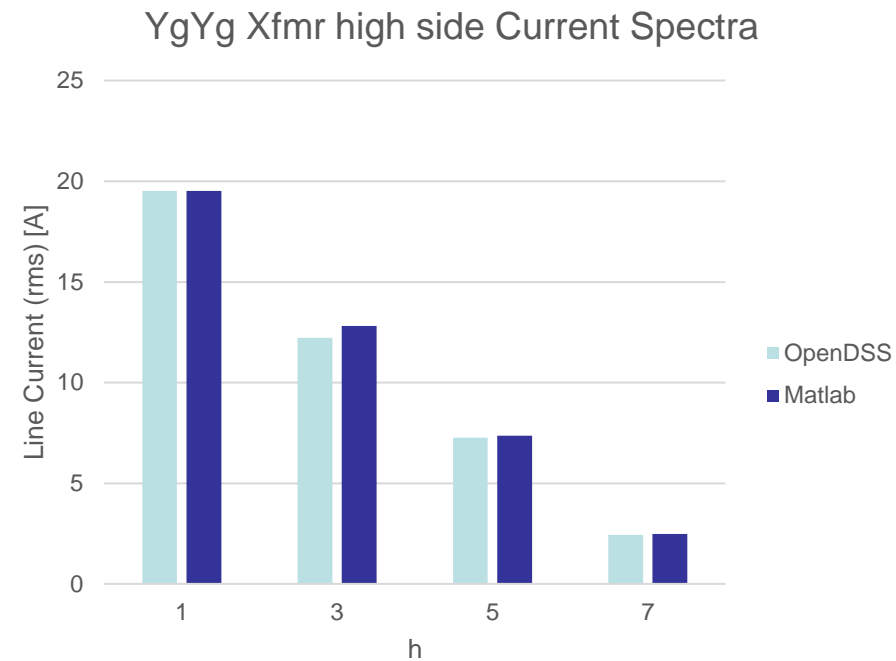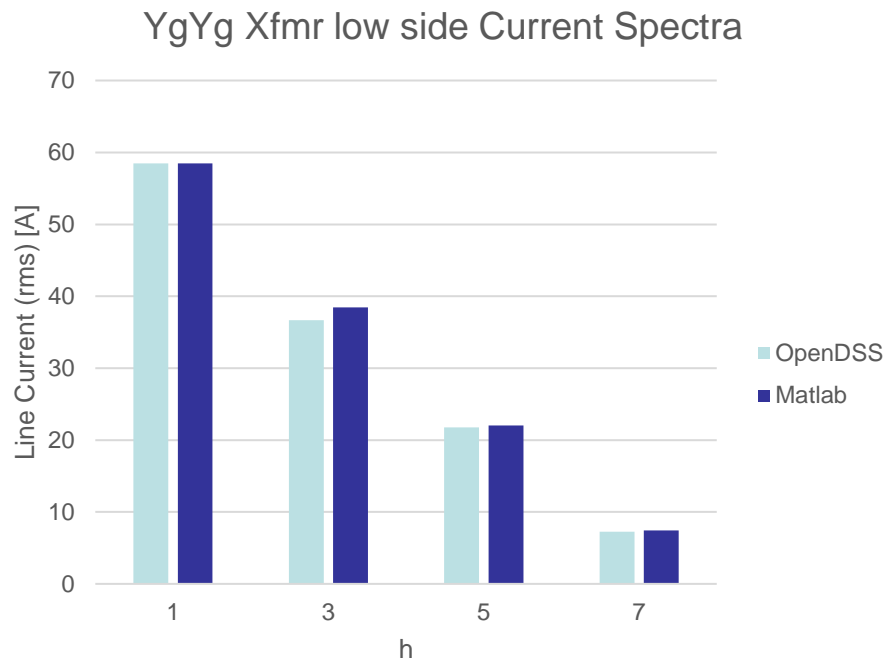
# Case study **B1**: IEEE 4 bus system with grounded wye-grounded wye (**YgYg**) Xfmr



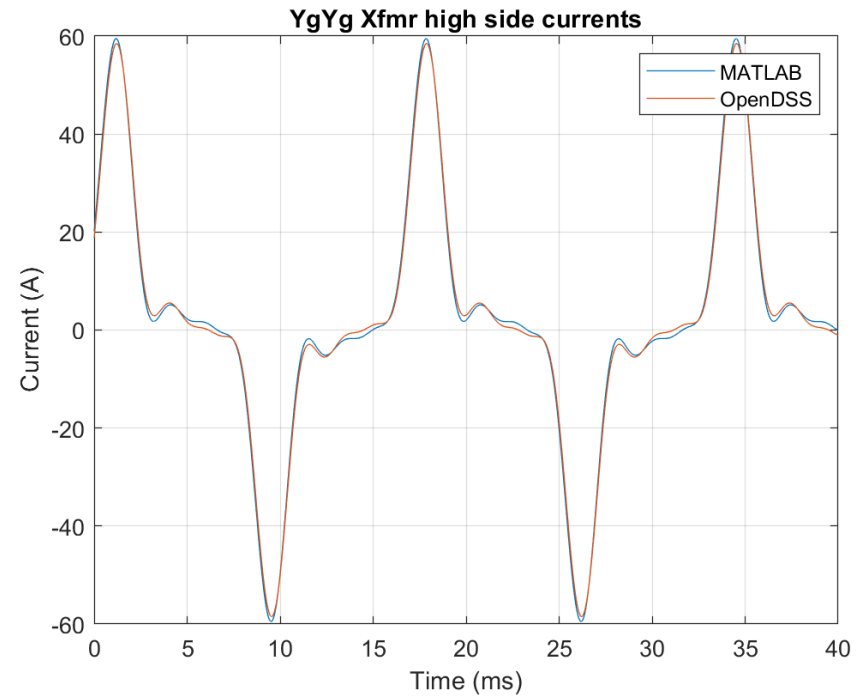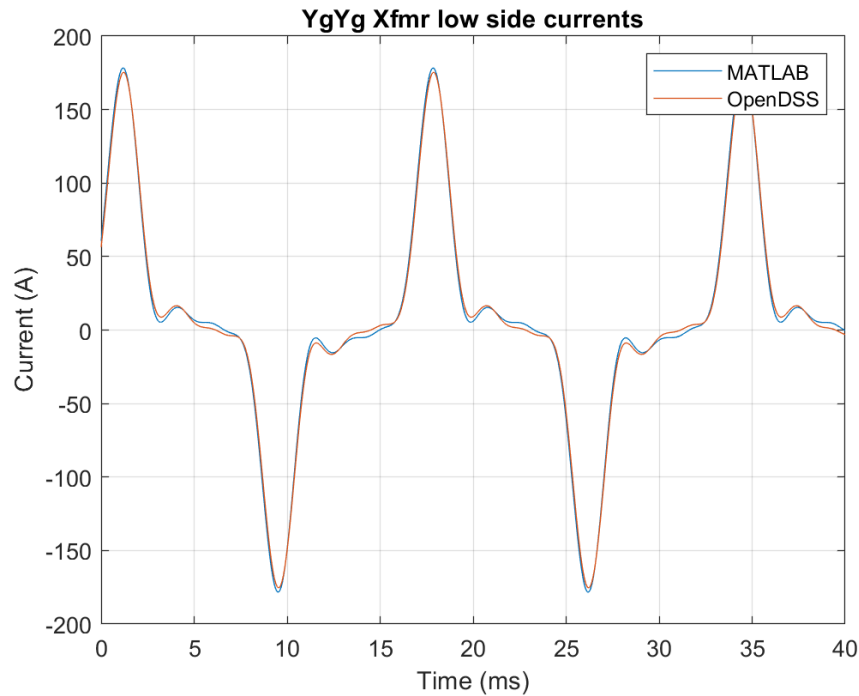
# Case study **B1**: IEEE 4 bus system with grounded wye-grounded wye (**YgYg**) Xfmr






# Case study **B1**: IEEE 4 bus system with grounded wye-grounded wye (**YgYg**) Xfmr



YgYg Xfmr low side Voltage Spectra

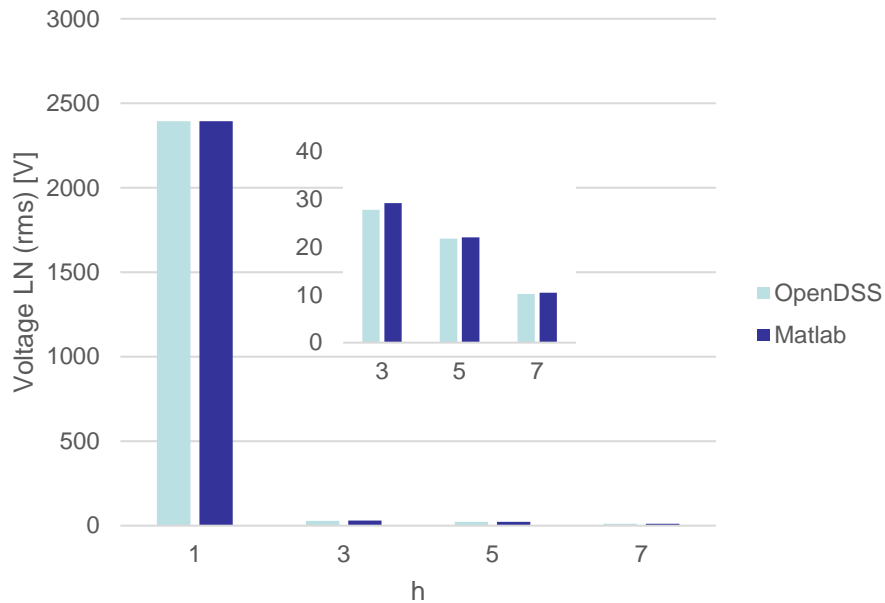

YgYg Xfmr high side Voltage Spectra


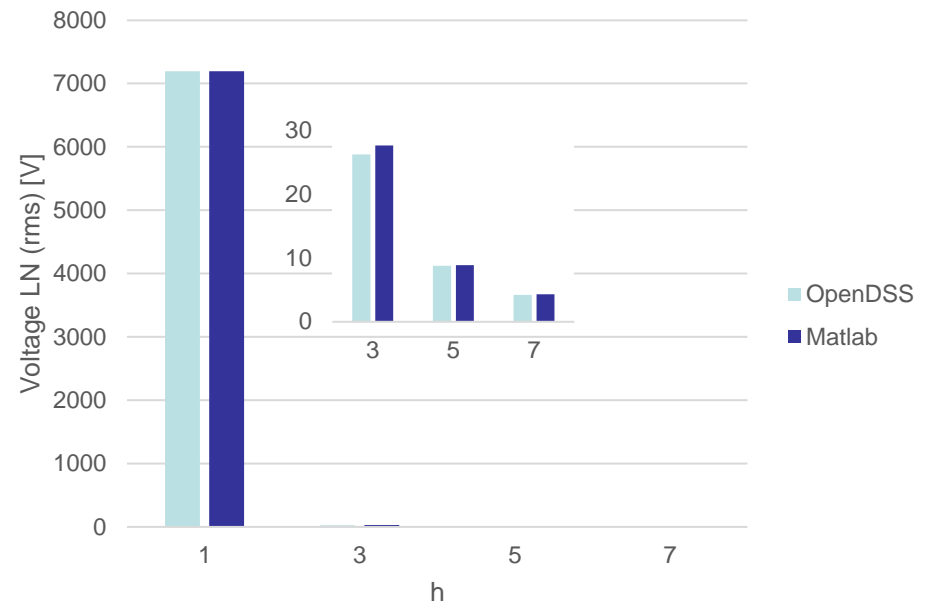

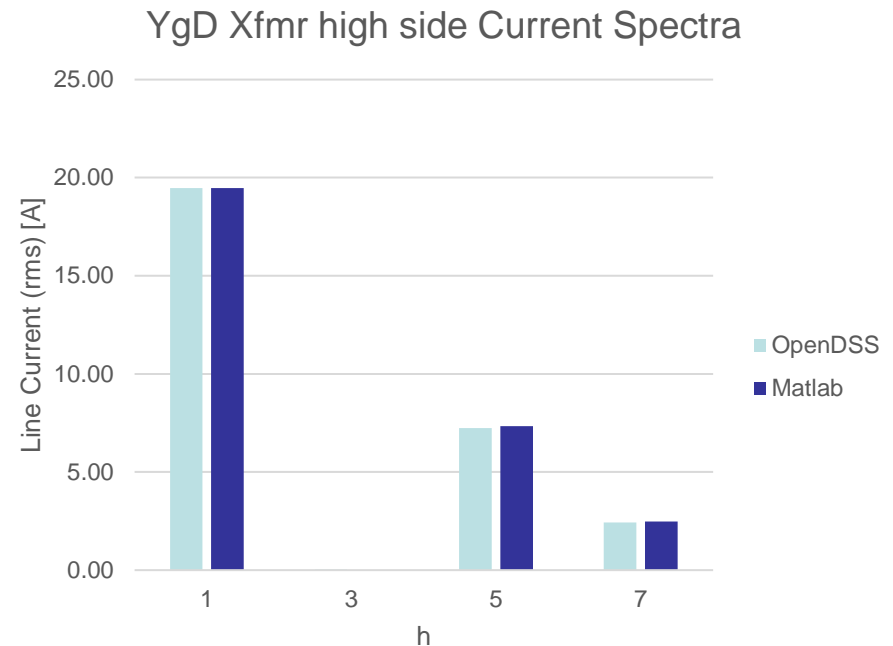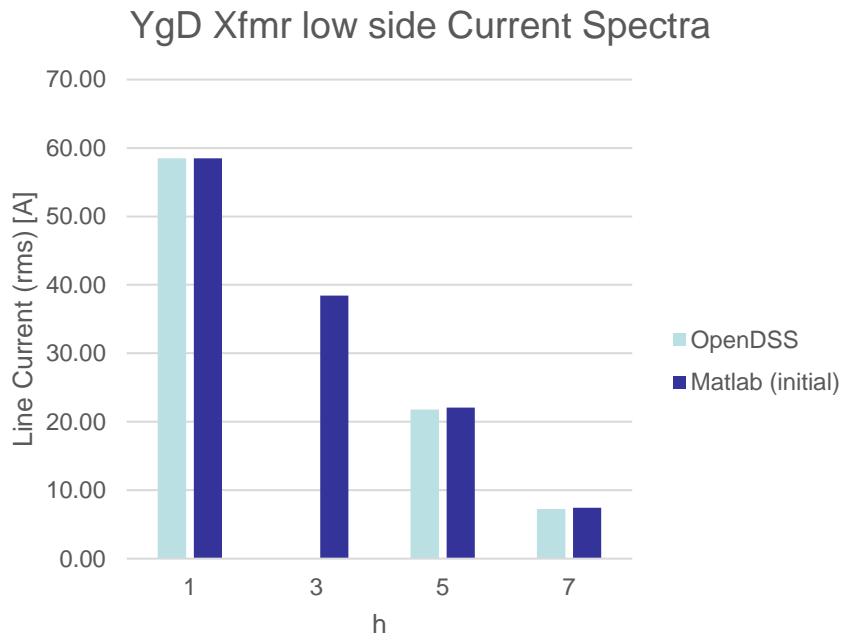
# Case study **B2**: IEEE 4 bus system with grounded wye-delta (**YgD**) Xfmr



The 3<sup>rd</sup> harmonic is inherently nullified by OpenDSS even on the low voltage (delta) side

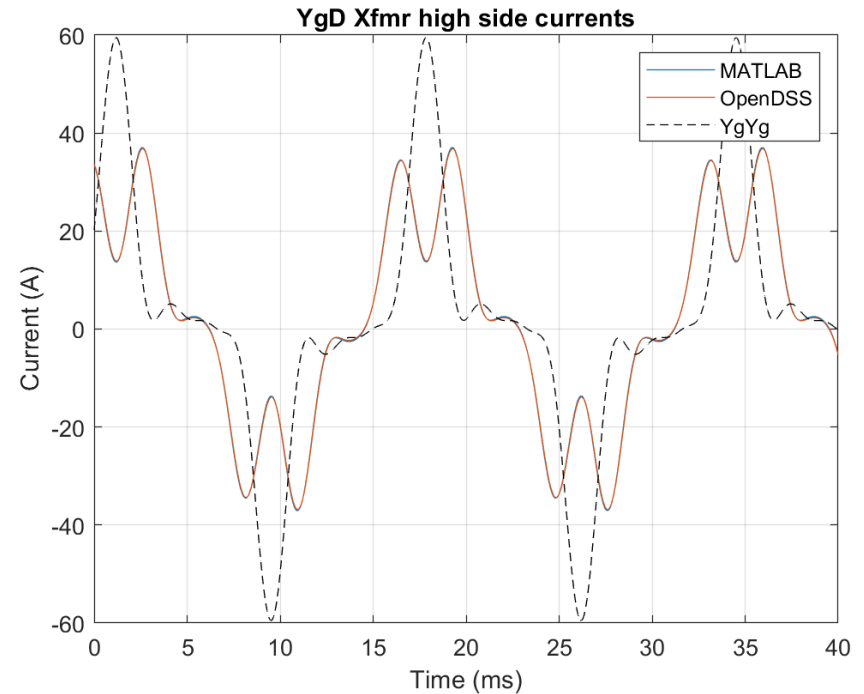
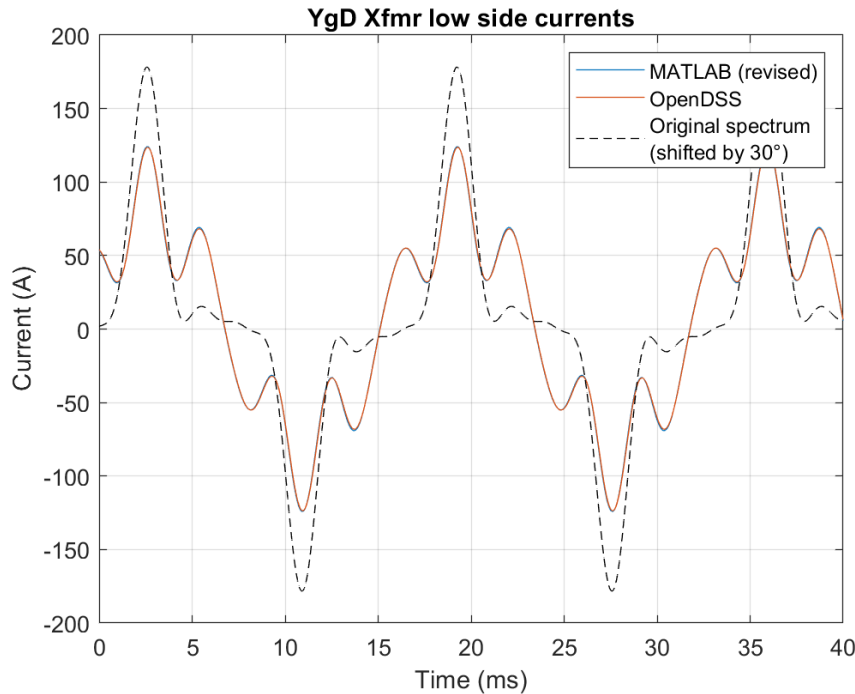
# Case study B2: IEEE 4 bus system with grounded wye-delta (YgD) Xfmr



Wave shape changes from low side to high side because of different phase sequences:



- Fundamental: shifted by  $+30^\circ$  from low to high side (positive sequence)
- 3<sup>rd</sup> harmonic: cancelled due to delta configuration (zero sequence)
- 5<sup>th</sup> harmonic: shifted by  $-30^\circ$  from low to high side (negative sequence)
- 7<sup>th</sup> harmonic: shifted by  $+30^\circ$  from low to high side (positive sequence)
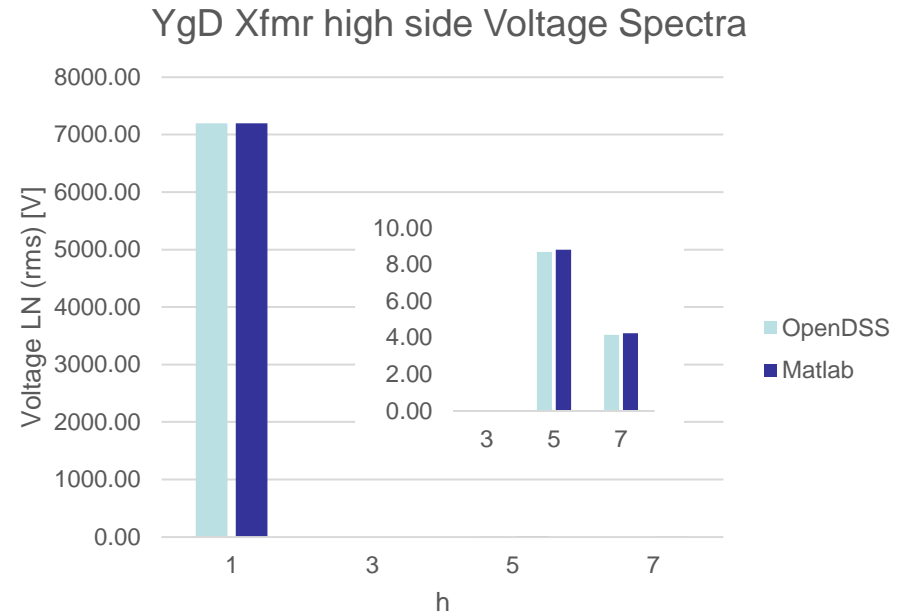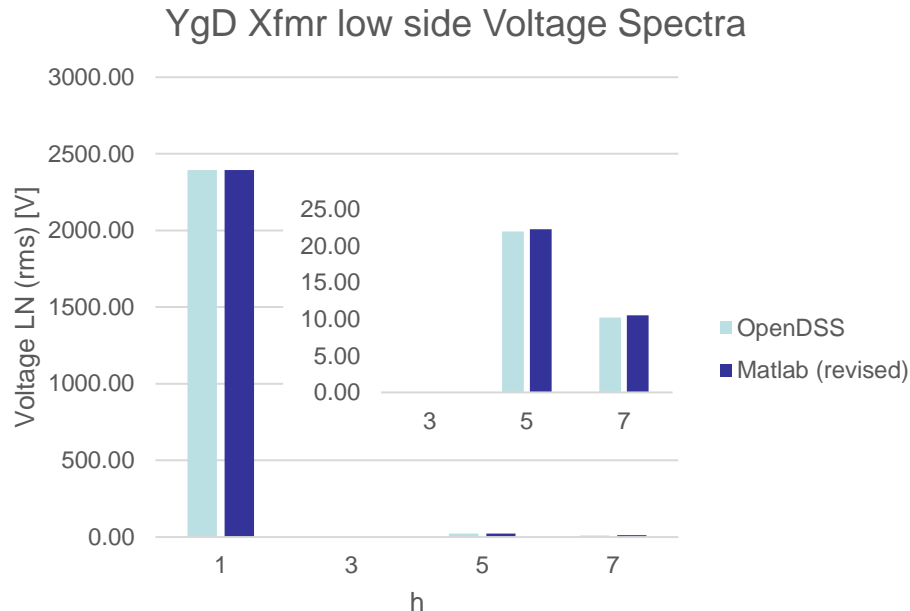
# Case study B2: IEEE 4 bus system with grounded wye-delta (YgD) Xfmr





The 3rd order harmonic current causes a sharp voltage resonance at the delta side of the Xfmr; this is due to the lack of a phase-to-ground path to drain the harmonic current. The 3<sup>rd</sup> harmonic voltage is excluded from the low side results due to its unrealistic magnitude.
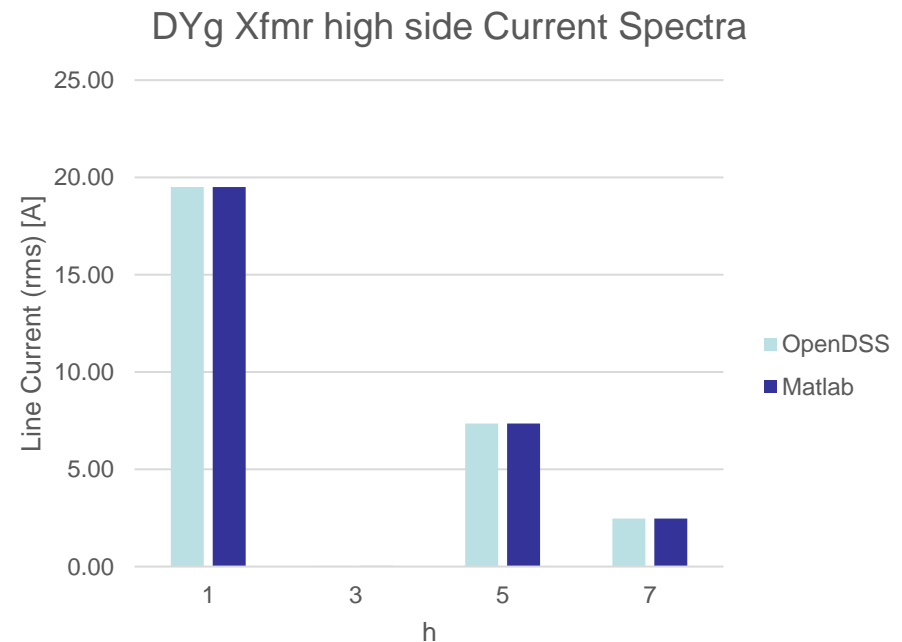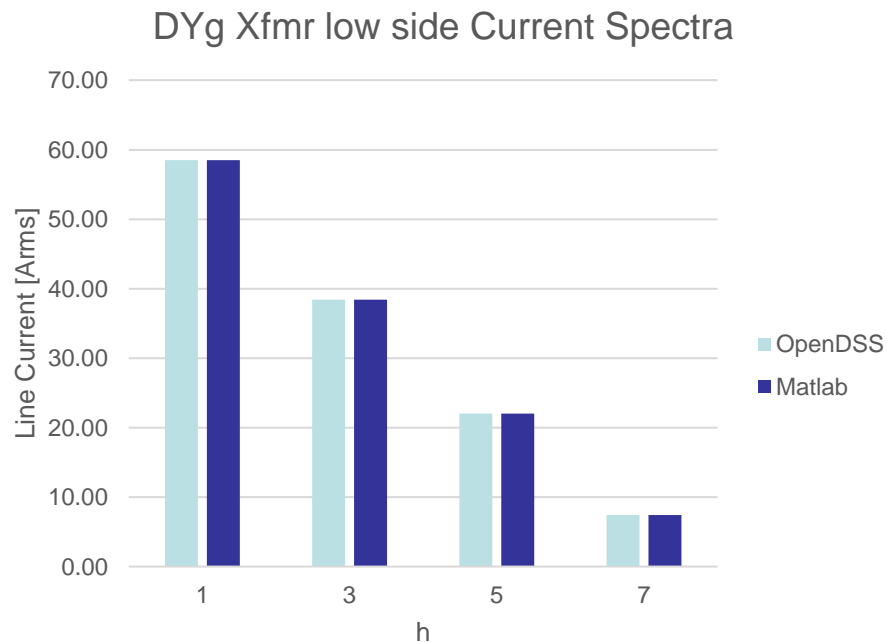
# Case study B3: IEEE 4 bus system with delta-grounded wye (DYg) Xfmr





The 3<sup>rd</sup> harmonic is **NOT** inherently nullified by OpenDSS on the low voltage (wye) side, unlike the YgD case
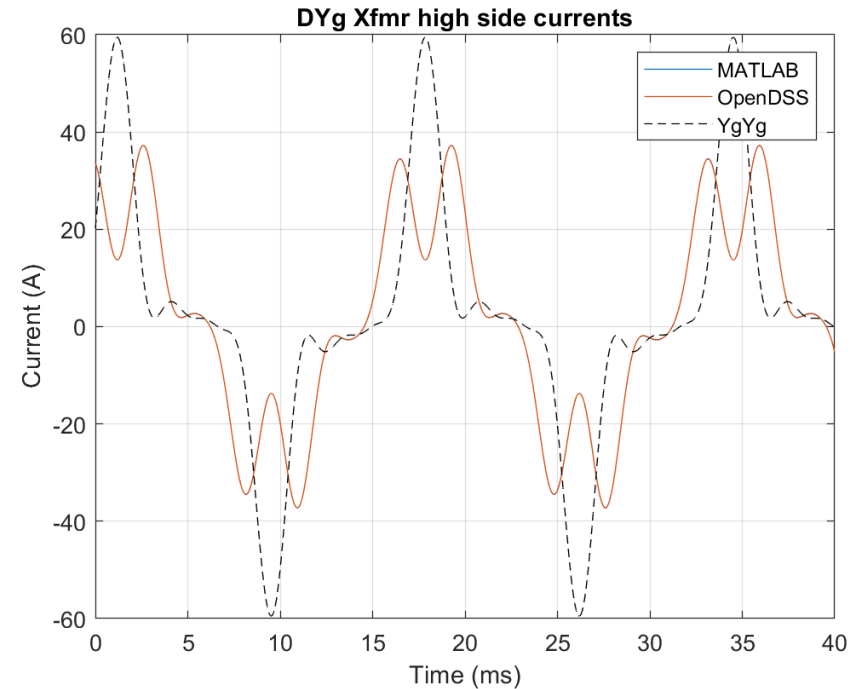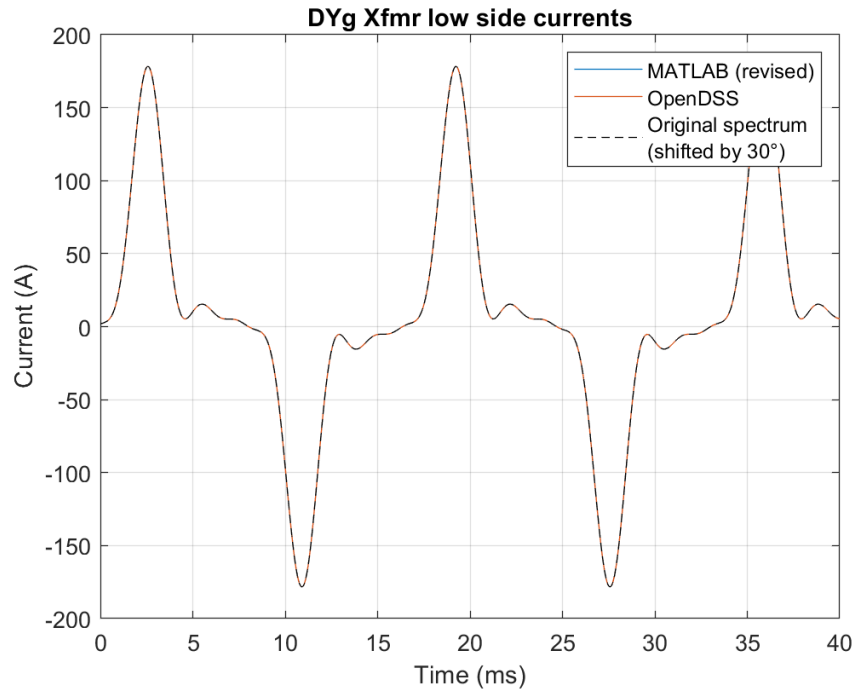
# Case study **B3**: IEEE 4 bus system with delta-grounded wye (**DYg**) Xfmr



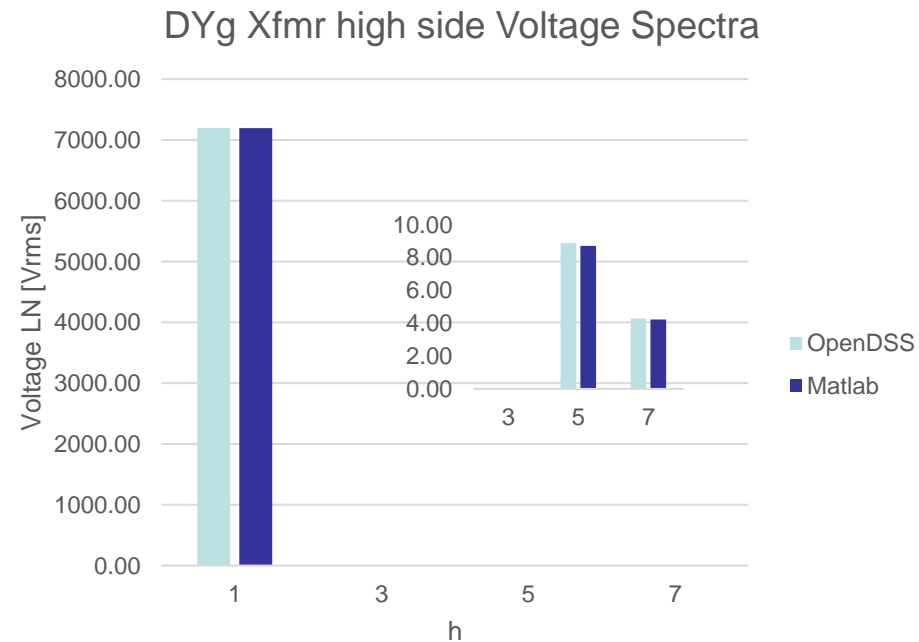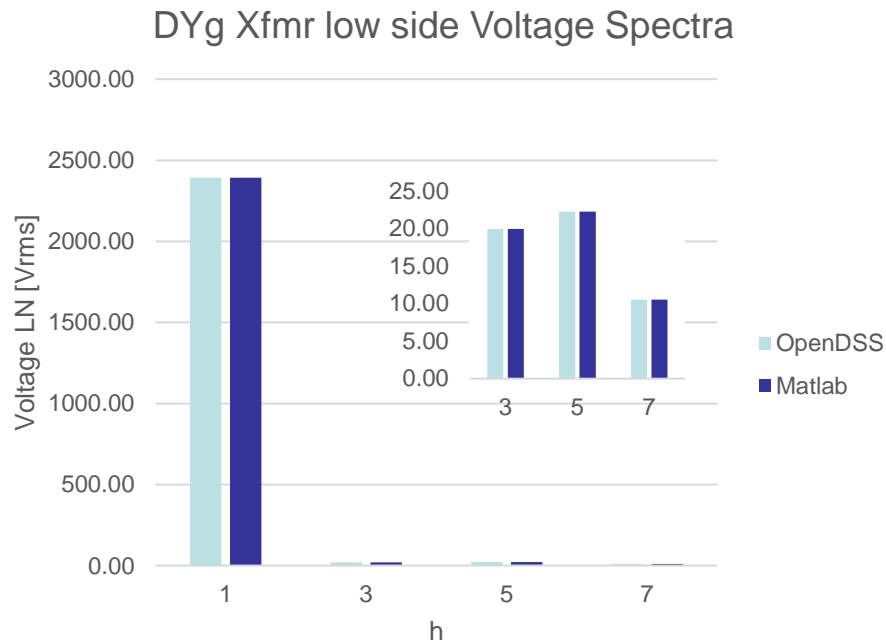
# Case study B3: IEEE 4 bus system with delta-grounded wye (DYg) Xfmr



# Case study C1: Inverter-Based Generation
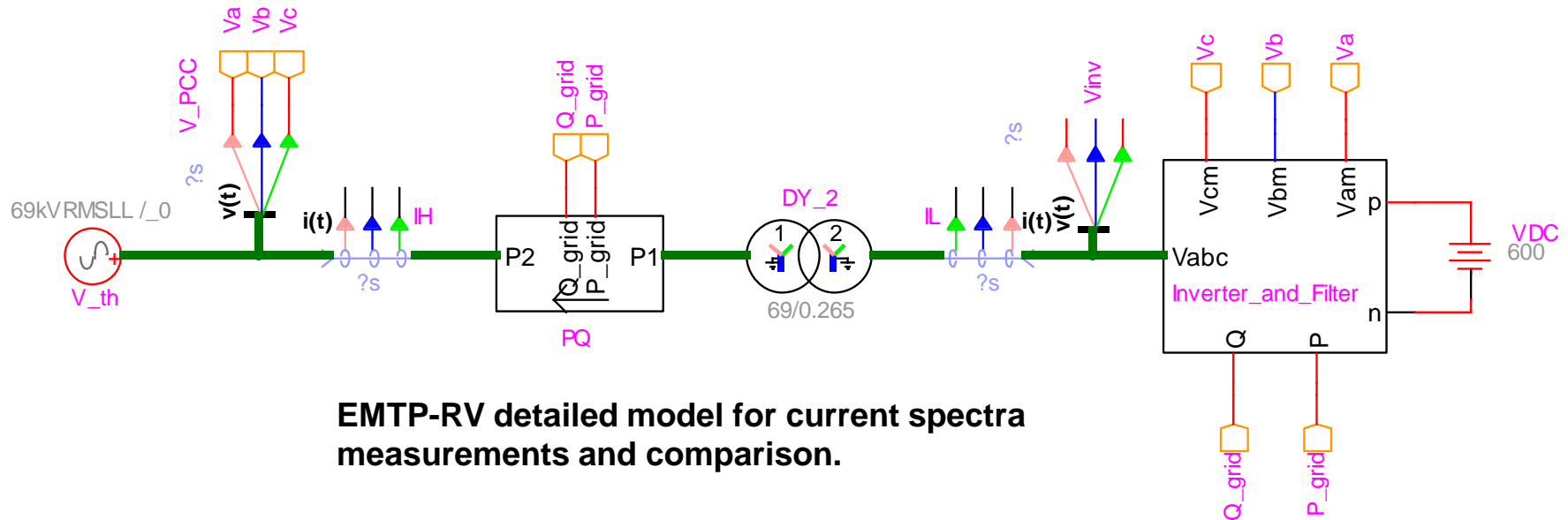
## Steady-State Harmonic Simulation - YgYg



**EMTP-RV detailed model for current spectra measurements and comparison.**

**IL – Low side Current Spectrum**

h	IRMS [A]	Phase [deg]
1	724.89659446	0.11621776
3	3.61852208	-86.18331333
5	60.59393845	123.78444976
7	0.60369343	153.70402571


The current spectrum for IL is obtained from the detailed model of a PV inverter involving power electronic switches




# Case study C1: Inverter-Based Generation

## Steady-State Harmonic Simulation – YgYg

YgYg Xfmr low side Current Spectra


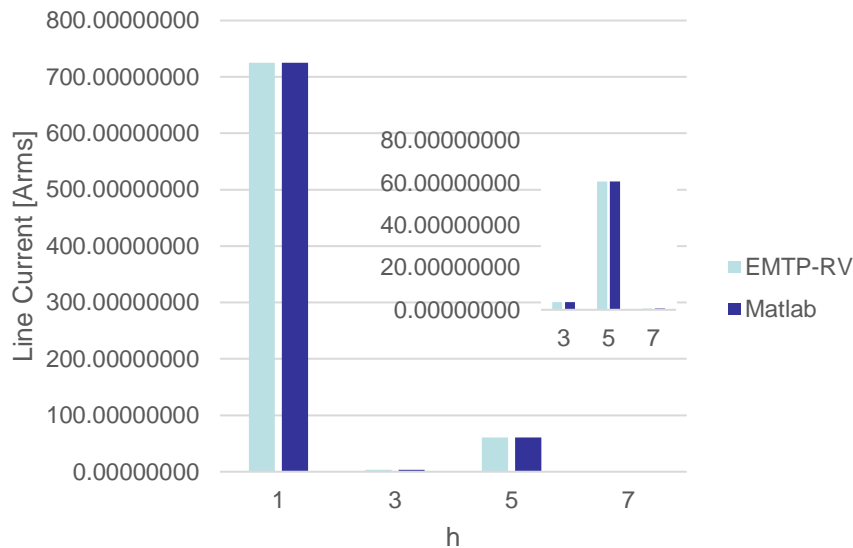


YgYg Xfmr high side Current Spectra

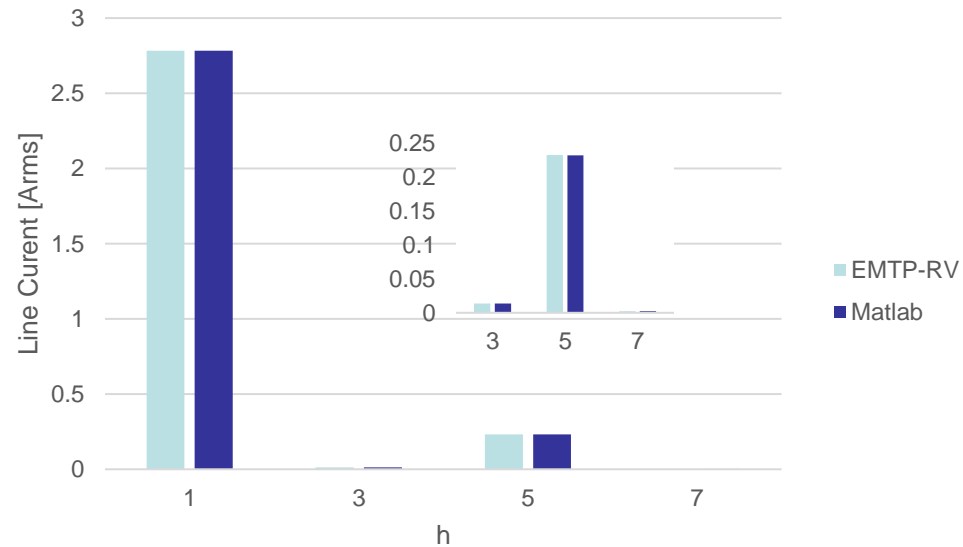

# Case study **C1**: Inverter-Based Generation
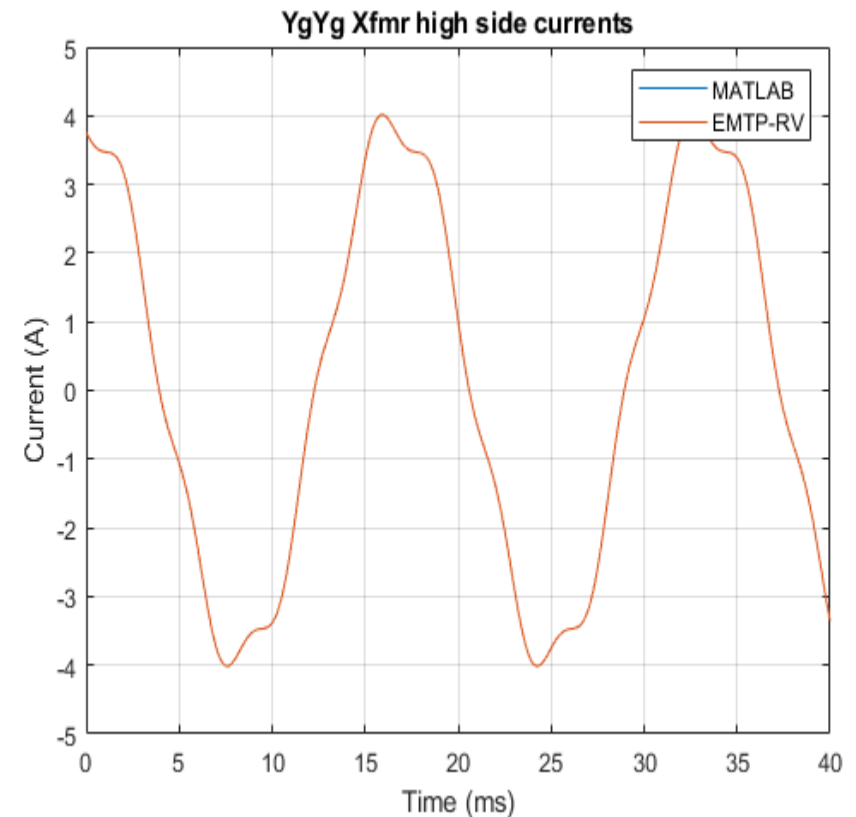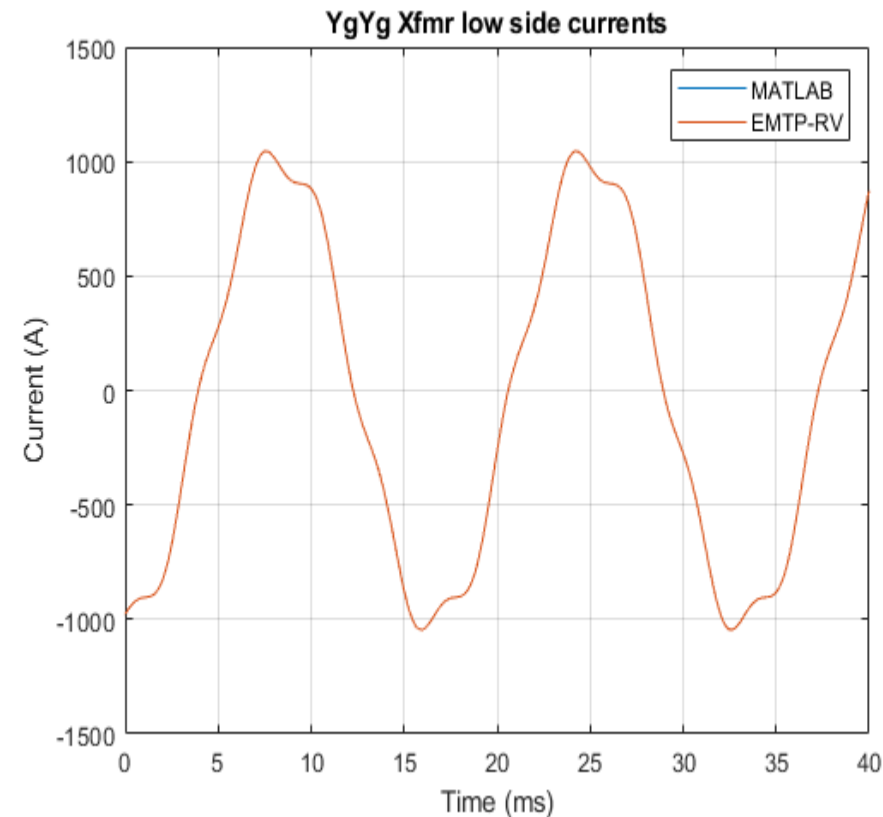
## Steady-State Harmonic Simulation – YgYg




Both currents waveshapes match very well – the MATLAB model is validated


# Case study C1: Inverter-Based Generation

## Steady-State Harmonic Simulation – YgYg

YgYg Xfmr low side Voltage Spectra

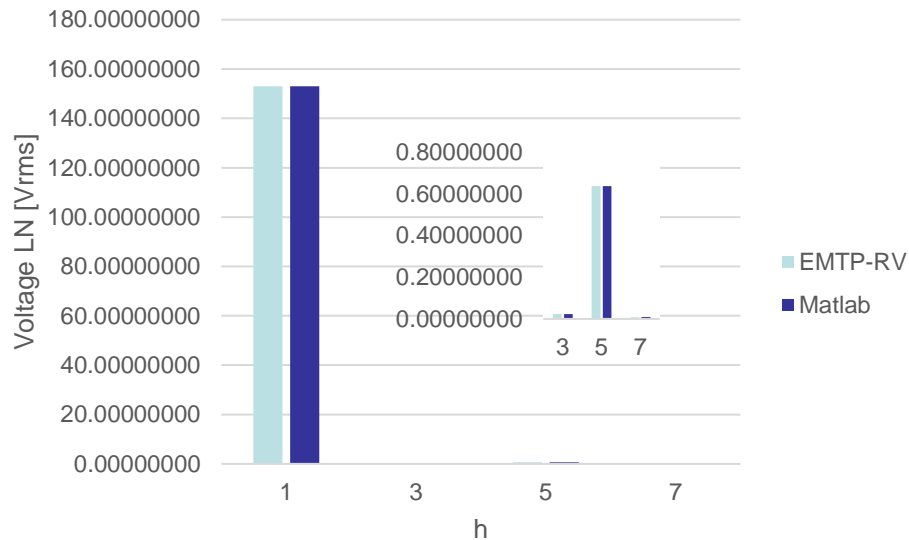


YgYg Xfmr high side Voltage Spectra

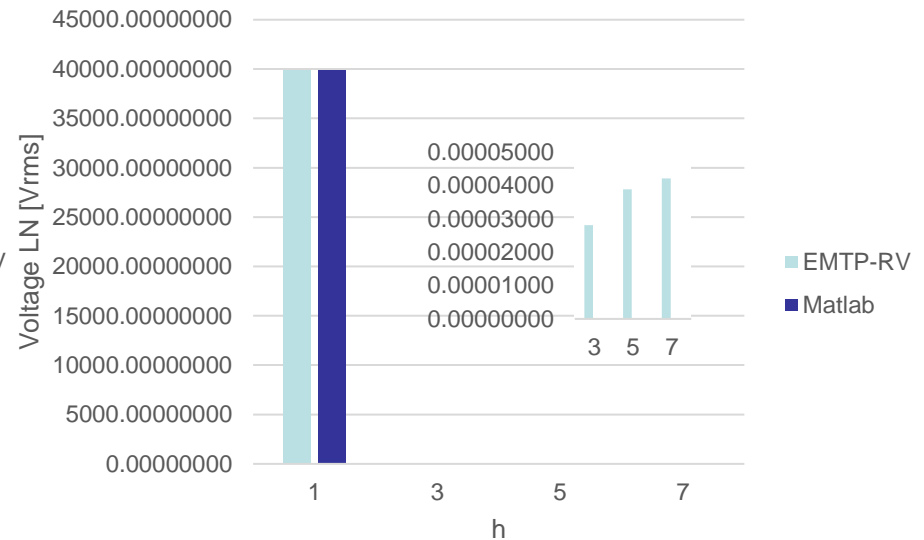

# Case study C2: Inverter-Based Generation
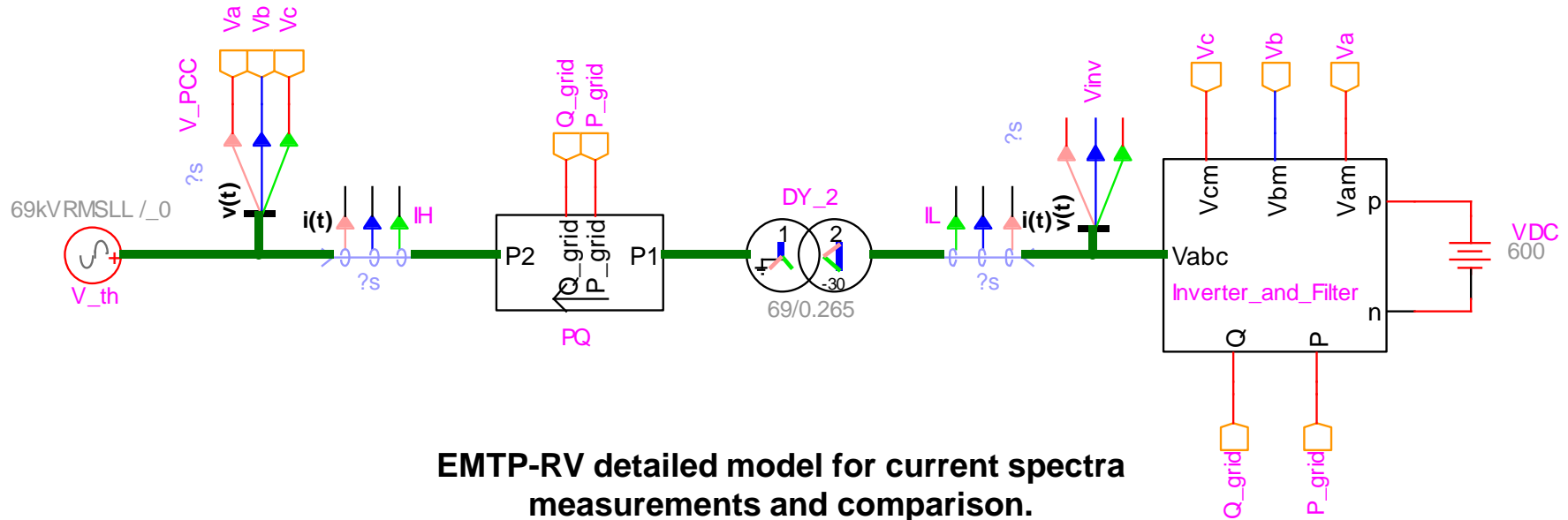
## Steady-State Harmonic Simulation – YgD




IL – Current Spectrum

h	IRMS [A]	Phase [deg]
1	725.49423181	-29.90098730
3	0.31181659	-98.22515297
5	36.88252625	-15.09932240
7	0.50247343	-54.64784741


# Case study C2: Inverter-Based Generation

## Steady-State Harmonic Simulation – YgD

YgD Xfmr low side Current Spectra

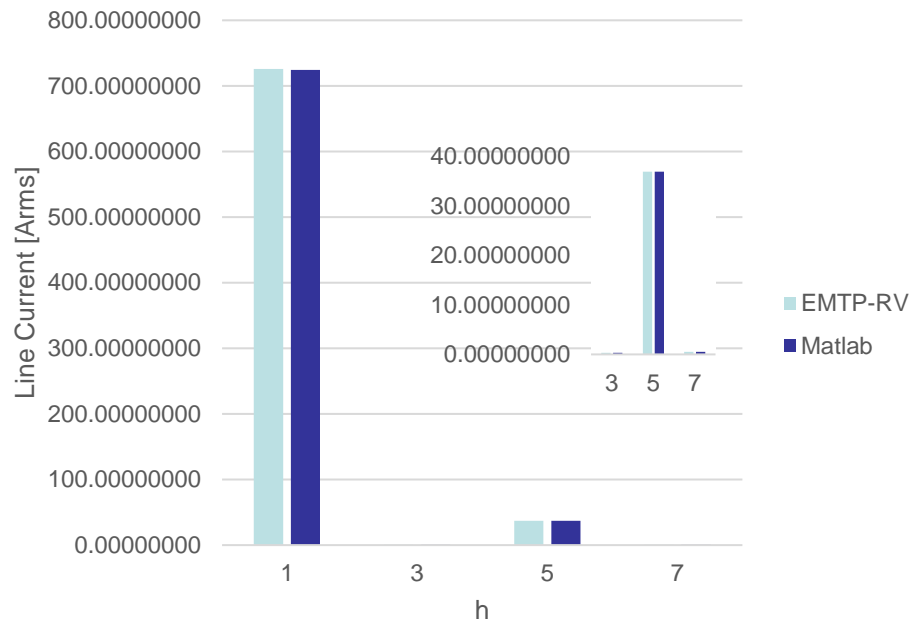



YgD Xfmr high side Current Spectra

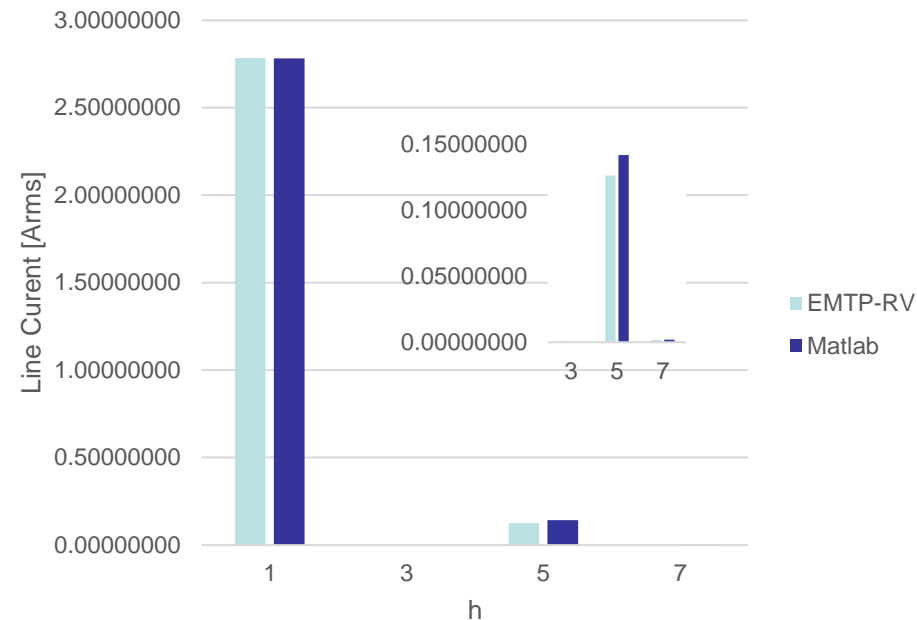

- Slightly different results obtained on the currents at the high side of the Xfmr
- The Matlab script assumes balanced conditions, whereas the EMTP-RV detailed model is inherently unbalanced

# Case study **C2**: Inverter-Based Generation

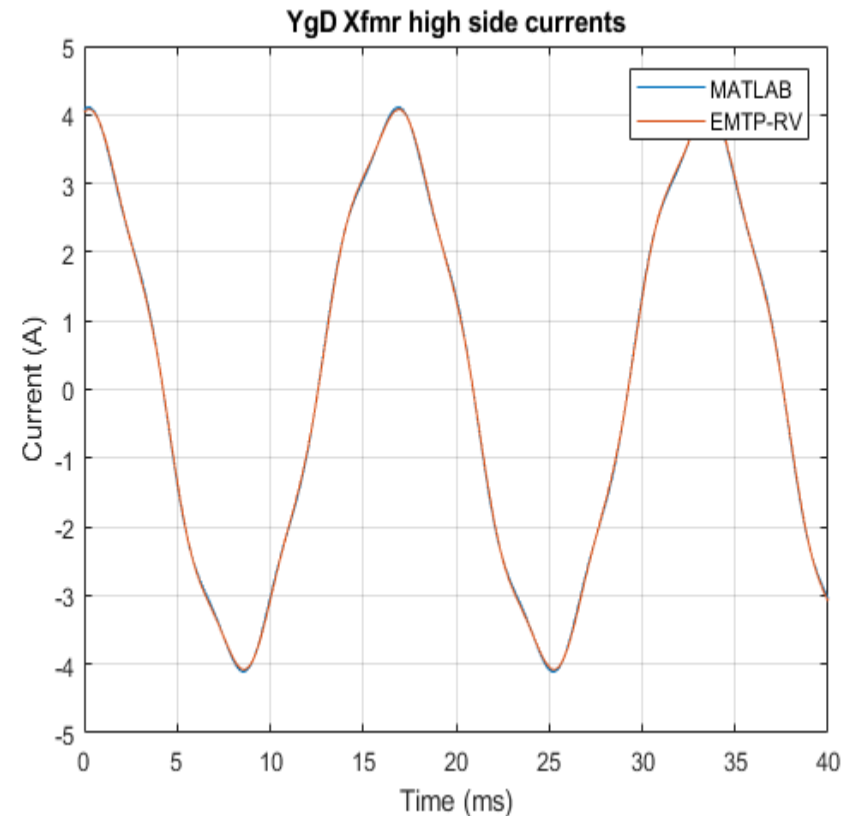
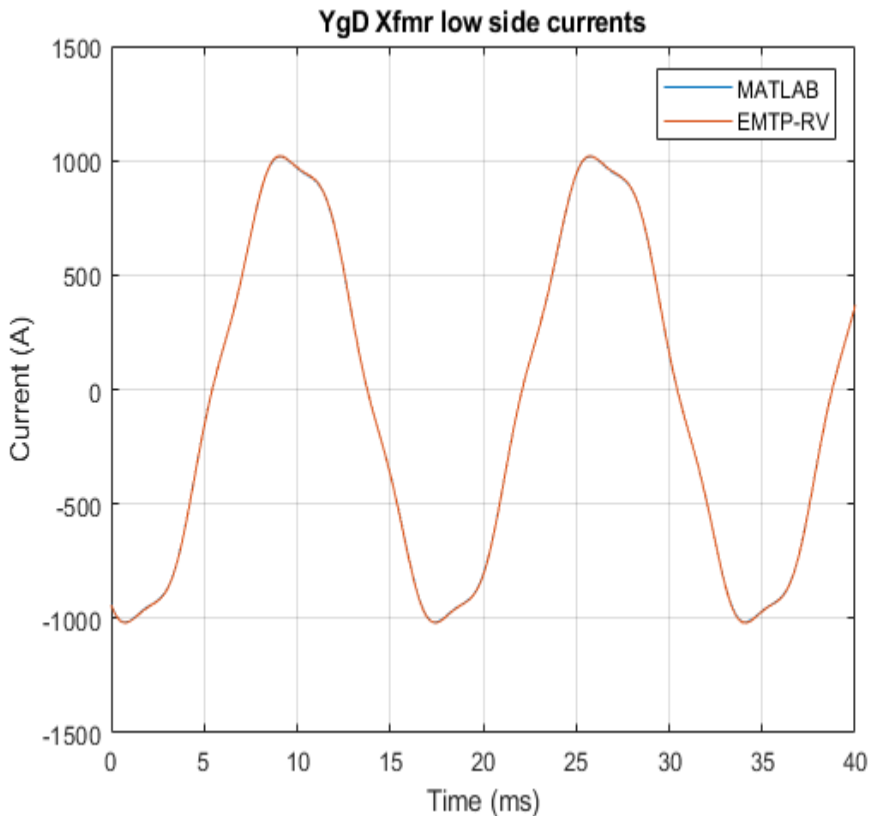
## Steady-State Harmonic Simulation – YgD



Both currents waveshapes match very well – the MATLAB model is validated

# Case study C2: Inverter-Based Generation
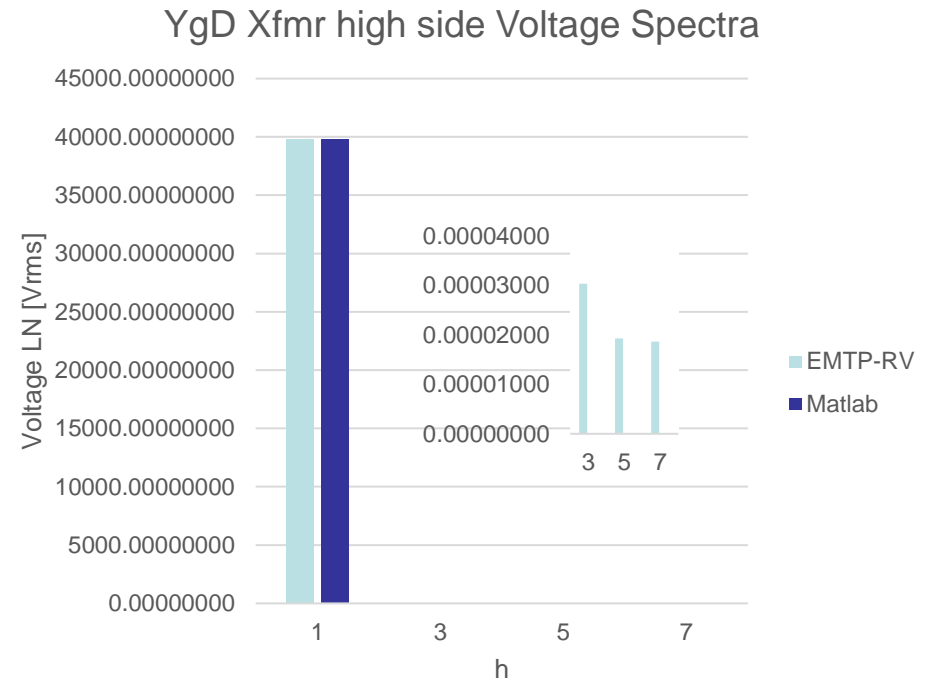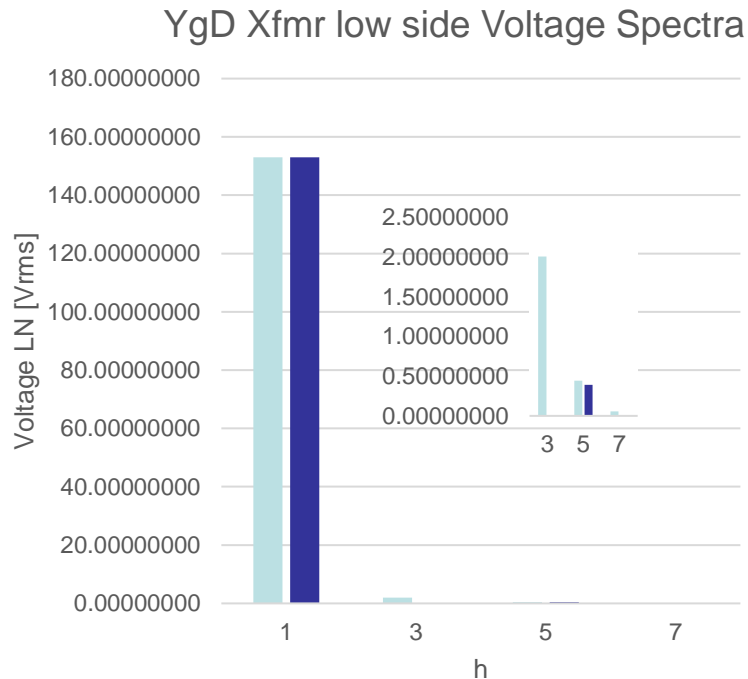
## Steady-State Harmonic Simulation – YgD



The EMTP-RV detailed model is inherently unbalanced, this causes the 3<sup>rd</sup> order harmonic to flow from low to high side of the Xfmr without causing a sharp voltage resonance. Matlab voltage results at the 3<sup>rd</sup> harmonic are excluded from the results due to its unrealistic magnitude.

# Conclusions

---

- Power system network models studied in class can successfully be expanded to simulate harmonic currents in steady-state. The  $Y_{\text{prim}}$  of each element requires adjustment depending on the harmonic frequency.
- Harmonic load-flow can be achieved by running separate simulations at each harmonic frequency, including the fundamental.
- YgYg Xfmr lets all harmonic currents flow through its windings.
- YgD Xfmr works as a filter for the triplen ( $3^{\text{rd}}$ ,  $6^{\text{th}}$ ,  $9^{\text{th}}$ ...) harmonic currents.
- Triplen harmonic currents cause a sharp voltage resonance in the delta side of a DYg/YgD Xfmr; this is due to the lack of a phase-to-ground path to drain the triplen harmonic currents.
- When triplen harmonic currents are injected in the wye side of a YgD/DYg Xfmr, the current can flow from the lines to the ground without causing a voltage resonance. No triplen harmonic current is observed in the delta side of the Xfmr since it is an open circuit for zero-sequence currents.